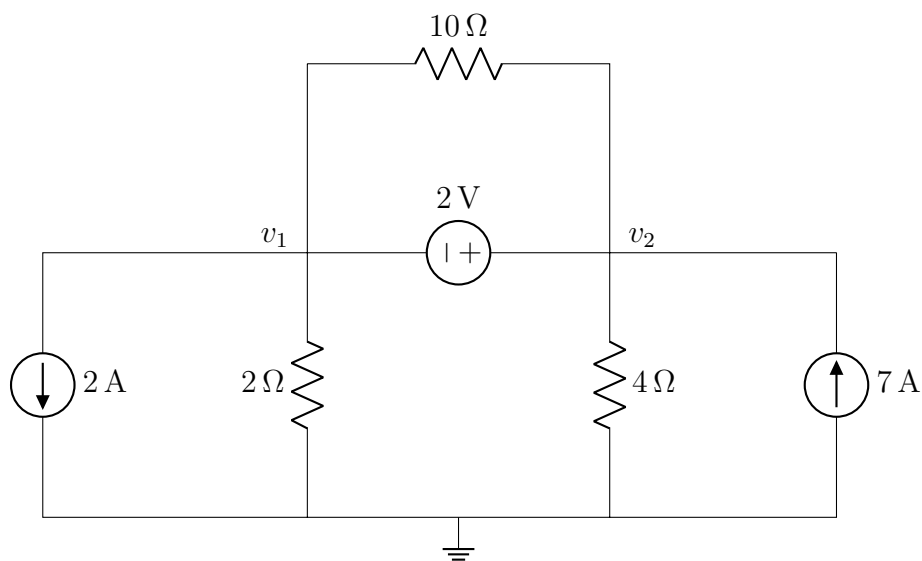



Semana 4 Nodos, Supernodos, Mallas y Supermallas

1. Encuentre v_1 y v_2





R/ $v_1 = 6\text{ V}$, $v_2 = 8\text{ V}$


2. Encontrar v_1 , v_2 y v_3 .

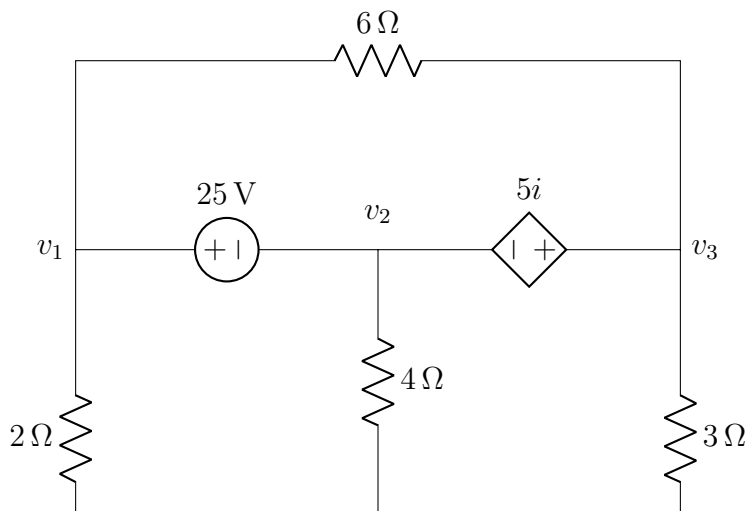

R/ $v_1 = 7,608\text{ V}$, $v_2 = 17,39\text{ V}$ y $v_3 = 1,6305\text{ V}$

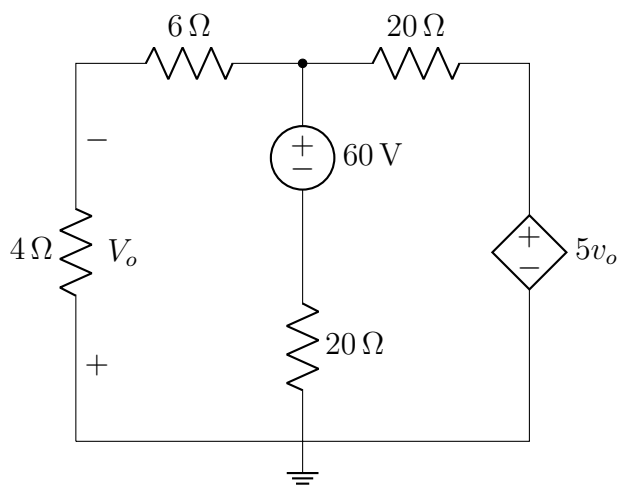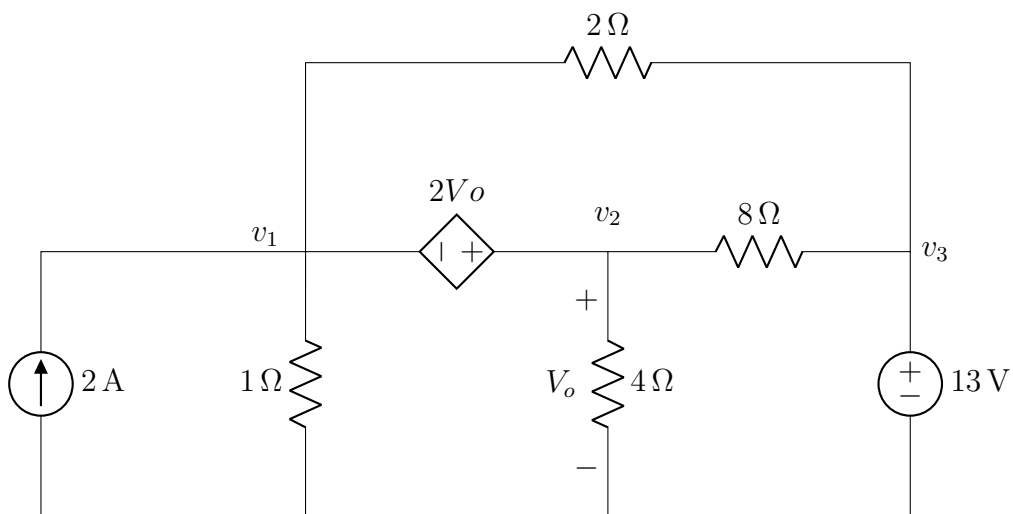
3. Encontrar V_o R/ $v_o = 12\text{ V}$ 4. Encontrar v_1 , v_2 y v_3 .R/ $v_1 = 18,86\text{ V}$, $v_2 = 6,29\text{ V}$ y $v_3 = 13\text{ V}$

5. Encontrar V_o e i_o .

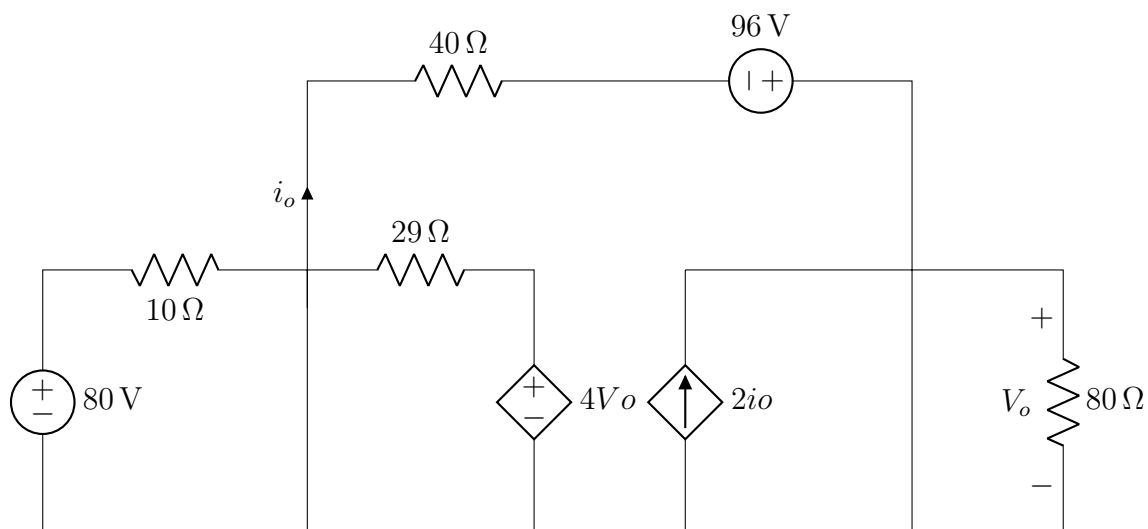


R/ $V_o = -1070\text{ V}, i_o = -4,48\text{ A}$

6. Hallar V_x e i_x en el circuito

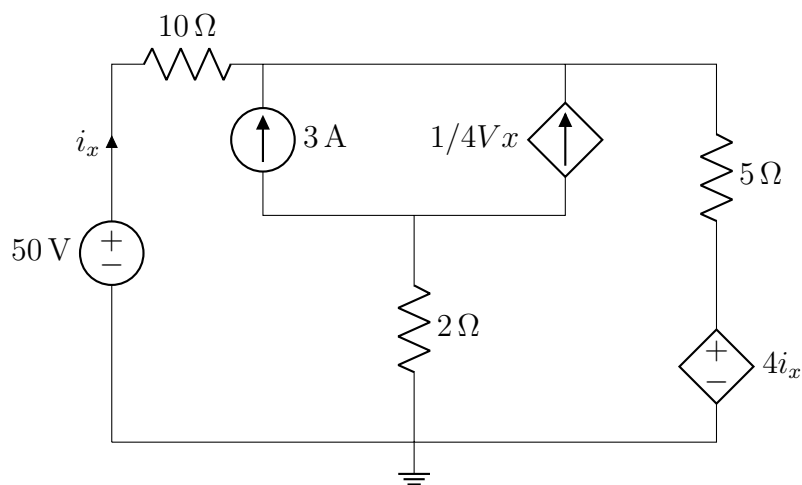


R/ $V_o = -4\text{ V}, i_o = 2,105\text{ A}$

7. Calcule V_o e i_o en el circuito.

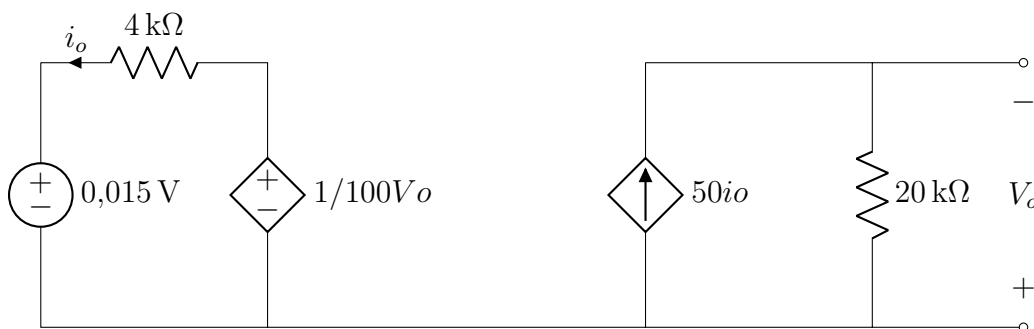

$$R / V_o = 2,5 \text{ V}, i_o = 2,5 \mu\text{A}$$

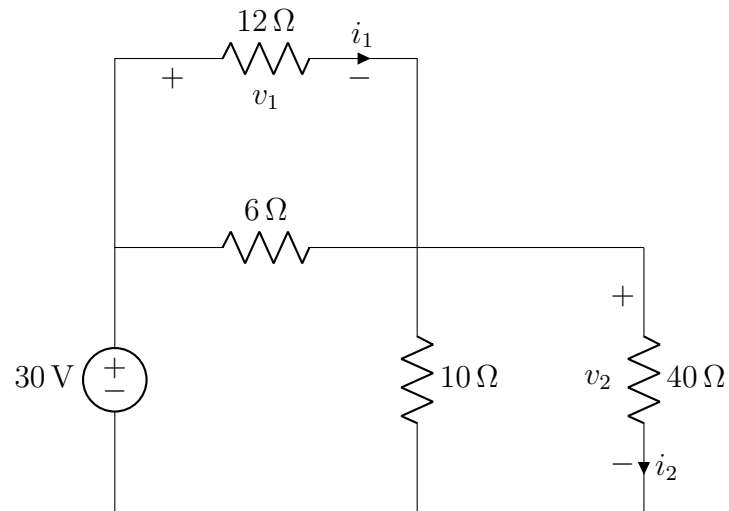8. Para el siguiente circuito encuentre i_1 e i_2 , v_1 y v_2 .



$$R / i_1 = 833,3 \text{ mA}, i_2 = 500 \text{ mA}, v_1 = 10 \text{ V}, v_2 = 20 \text{ V}$$